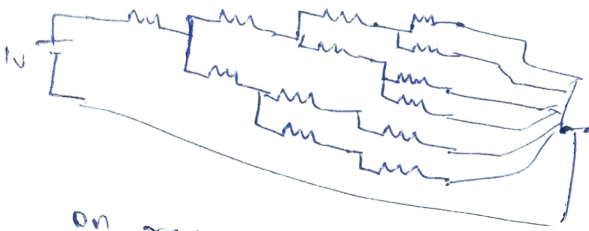


Problem set 2


Hemanth, N
2019503519

①




on reducing, the resistance halves, since they are in parallel.

\Rightarrow

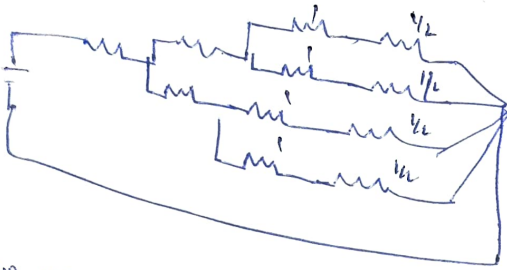

on reducing the next immediate pair, it becomes $1 + 1/2 = \underline{\underline{3/2 \Omega}}$

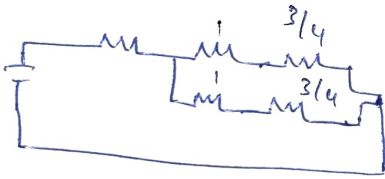
continuing reduction, $\underline{\underline{3/4 \Omega}}$



$$1 + 3/4 = \underline{\underline{7/4}}$$

two $7/4 \Omega$ in "||"
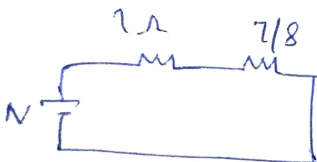
$$\Rightarrow R_{eq} = \underline{\underline{7/8 \Omega}}$$




Finally, since these are in series $1 + 7/8$

$$\Rightarrow \boxed{R_{eq} = \underline{\underline{15/8 \Omega}}}$$


$$i = V/R \Rightarrow i = V/15/8 \Rightarrow \frac{18}{5} A = \underline{\underline{0.533 A}}$$

$$\boxed{R_{eq} = \underline{\underline{15/8 \Omega}}, i = \underline{\underline{0.533 A}}}$$


(2)

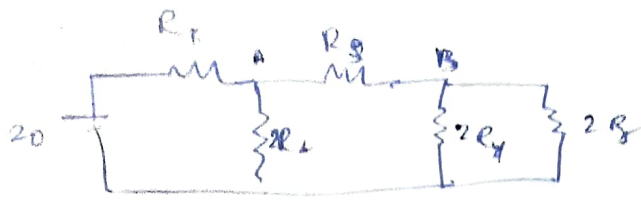14 March N
2019 503519
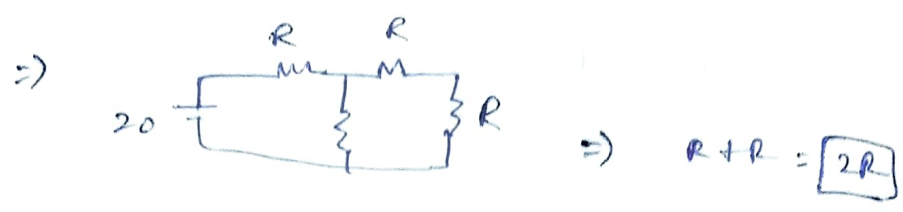
$$R_{eq} = \frac{2R \times 2R}{4R} = \boxed{R}$$



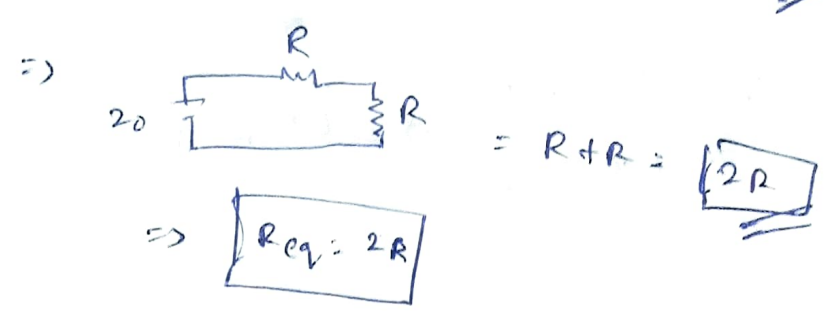
$$I = \frac{20}{2R + 2R} = \boxed{\frac{5}{R}}$$



$$V = 20 \Rightarrow I = \frac{20}{2R} = 10/R$$

$$I_{at 2R} = \frac{10/R \times 2R}{2R + 2R} = 10/R + \frac{2R}{4R}$$
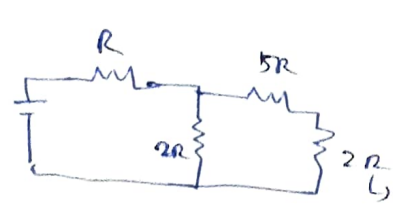
$$\Rightarrow \boxed{I_{2R} = \frac{5}{R}}$$



$$I = \frac{5/R \times 2R}{4R} = \boxed{\frac{5}{2R}}$$

$$Power = 12.5 = \left(\frac{5}{2R}\right)^2 \times R$$

$$\Rightarrow \frac{25}{4R} \times R = 12.5$$

$$\Rightarrow \boxed{R = 0.5 \Omega}$$

$$\textcircled{*} \text{ Total Power} = \frac{10}{R} \times 2R = \underline{\underline{20W}}$$

$$\textcircled{*} V_{at R} = \frac{10}{0.5} \times 0.5 = \underline{\underline{10V}}$$

$$I = \frac{10}{0.5} = \frac{20}{1} = \underline{\underline{20A}}$$

$$P = (20)^2 \cdot 0.5 \quad [P = I^2 \cdot R]$$

$$\Rightarrow \underline{\underline{P = 200W}}$$

$$\textcircled{+} V_{at \text{ second } R} = \frac{5}{R} \times R = \underline{\underline{5V}}$$

$$\boxed{I = 10A} \quad (I = V/R \Rightarrow 5/0.5)$$

$$\Rightarrow P = (10^2) \cdot 0.5 = 50$$

$$\therefore \boxed{P = 50W}$$

$$\textcircled{A} V_{at 2R} = \frac{5}{R} \times 2R = 10V$$

$$I_{at 2R} = \frac{5}{0.5} = \underline{\underline{10A}}$$


$$P_{at 2R} = \left(\frac{5}{R}\right)^2 \cdot 2R = \frac{10}{R} = \frac{10}{0.5}$$

$$\boxed{P_{at 2R} = 20W}$$


$$\textcircled{+} V_{at \text{ second } 2R} = \frac{5}{2R} \times 2R = \underline{\underline{5V}} ; \Rightarrow I = \frac{5}{2 \times 0.5} = \underline{\underline{5A}}$$

$$P_{at 2R} = (5)^2 \cdot 0.5 = \underline{\underline{12.5W}}$$

(3)

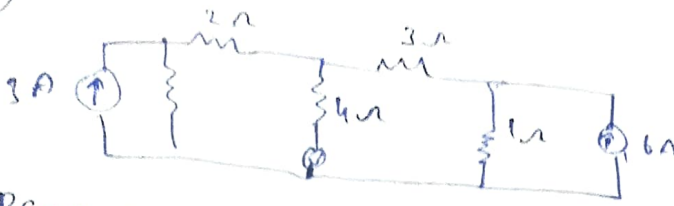


Remove 6V & 6A source

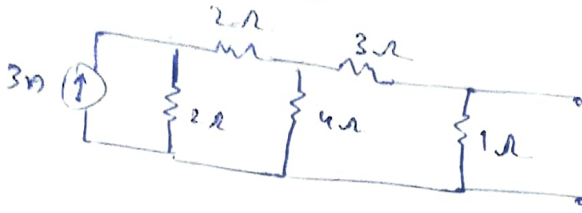

①

⇒

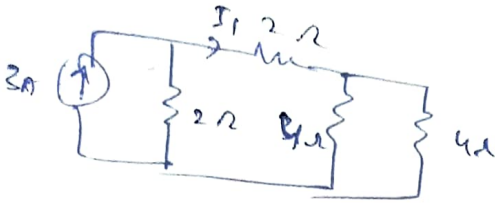

②

⇒



③

⇒



④

↓

$$I_{2\Omega} = \frac{4(3)}{6} = 2A$$


$$I_{4\Omega} = 3 - 2 = 1A$$


from ② ⇒

$I_{4\Omega}$ current thro, will divide into 2 equal branch ⇒ current thro both resistors are same

$$\Rightarrow \underline{I_{4\Omega} = 0.5A} \downarrow$$

Remove 3A & 6A



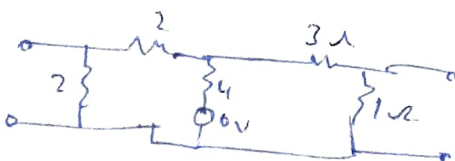


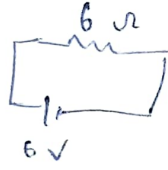

$$I_2 = V/R = 6/6$$

$$I_2 = 1A \text{ upward}$$

remove 3A & 6V

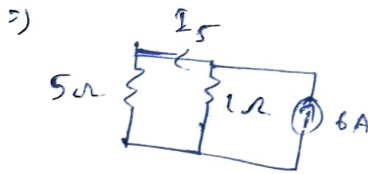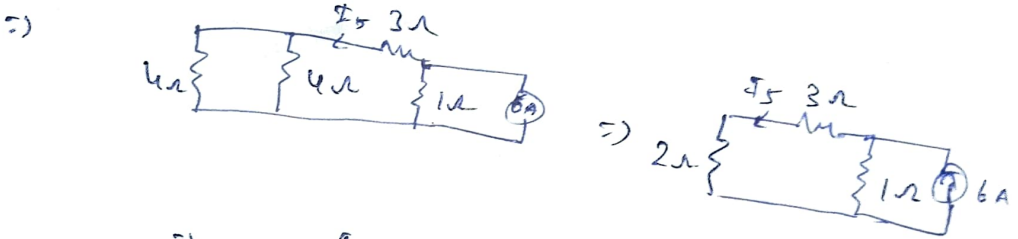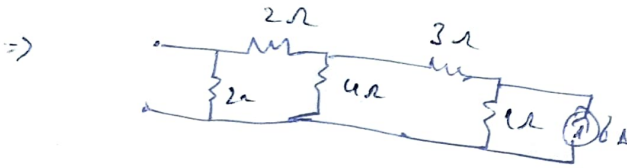

$$I_{5\Omega} = \frac{1 \times 6}{6} = \underline{1A}$$

from 2nd diag, $I_{5\Omega}$ it is clear, that $I_{5\Omega}$ will divide into equal branch currents $0.5A$ & $0.5A$

$$\underline{I_{4\Omega} = 0.5A \text{ downward}}$$


$$I_T = 0.5 + 0.5 =$$

$$= \underline{0A}$$

$$\left(\begin{array}{l} 0.5 \text{ down, } 0.5 \text{ down} \\ 1A \text{ upward} \end{array} \right)$$

$$\underline{I_T = 0A}$$


(4)

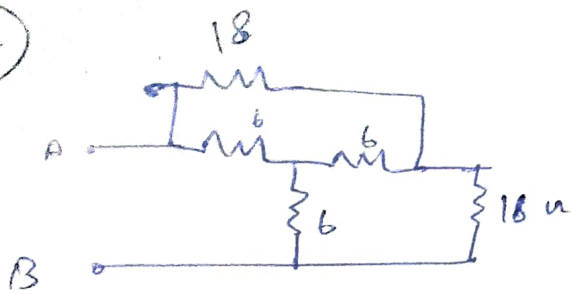

Star to Delta \Rightarrow R values are same \Rightarrow


3R

$$\therefore 3 \times 6 = 18 \Omega$$

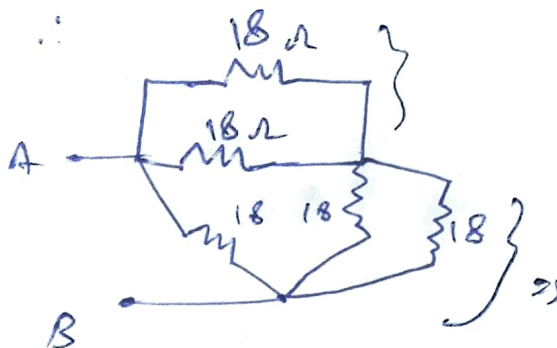


$$\frac{18 \times 18}{36} = 9 \Omega$$

\Rightarrow

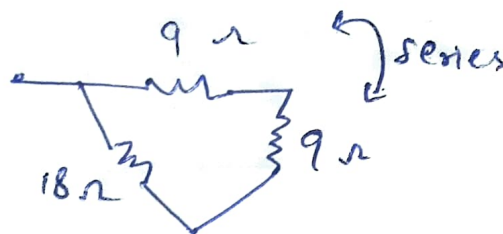

$$\Rightarrow 9 + 9 = 18 \Omega$$


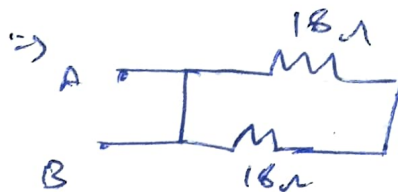


$$\Rightarrow \frac{18(18)}{18+18} = 9 \Omega$$

So overall resistance across AB

$$R_{eq} = 9 \Omega$$

Hemant, N
2019503519

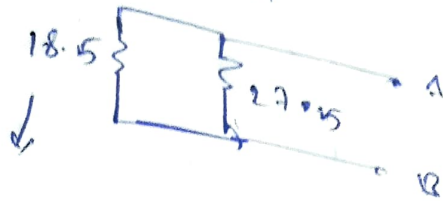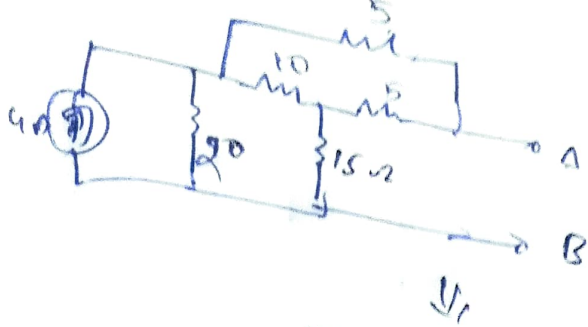


$$I_{18.5} = \frac{27.05}{46} \times 4 = \underline{\underline{2.39A}}$$

$$(R_{Th} = 11.09 \Omega)$$

$$V_{18.56} = 18.56 \times 2.39 = \underline{\underline{44.35V}}$$

=)

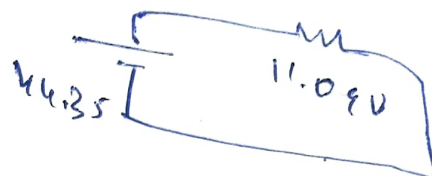

$$\begin{cases} R_{Th} = 11.09 \Omega \\ V_{Th} = 44.35 V \end{cases}$$

$$\text{Power} = \frac{V_{Th}^2}{4 R_{Th}}$$

$$= \frac{1966.92}{44.38}$$

$$\boxed{\text{Power} = 44.32 V}$$